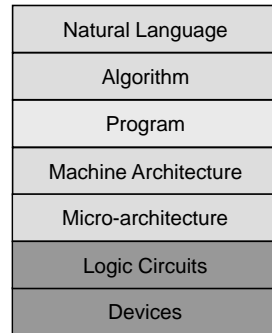


These notes are Dr Delmas' and many other people's notes

## Chapter 3

### Digital Logic Structures



COMPSCI 210

1

## The Building Blocks of Computers

- Logic gates are the basic building blocks of computers
  - AND, NOT, ...
- Combining the logic functions together, higher-level structures can be built
  - Adder, multiplexer, decoder, register, ...
- A processor can be built from the circuits providing higher-level functions

COMPSCI 210

2

## Agenda & Reading

- Logic gates
- Simple logic circuits
- Read Chapter 3 of the textbook

COMPSCI 210

3

## Agenda


- **Logic gates**
  - **The functionality of logic gates**
  - **How to convert a logic expression into an expression that contains NOT, NOR and NAND operators only**
- Simple logic circuits

COMPSCI 210

4




## NOR Gate

 

COMPSCI 210

9


## AND Gate

 

COMPSCI 210

10

## NAND Gate

 

COMPSCI 210

11


## DeMorgan's Law (1)

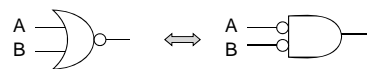
- NAND, NOR, NOT are the three types of gates for building logic circuits
- When designing a logic circuit, it is more convenient to use AND, OR, NOT in the design.
- Before a design is sent to the factory for fabrication, the design needs to be converted to a design that consists of NAND, NOR, NOT gates only
- The conversion is carried out using the DeMorgan's Law

COMPSCI 210

12

## DeMorgan's Law (2)

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$


$$\overline{A + B} = \bar{A} \cdot \bar{B}$$


COMPSCI 210

13

## DeMorgan's Law (3)

- To apply the DeMorgan Law to convert a circuit, you can first apply the invert operation twice to the expression that you want to convert

$$A \cdot B = \overline{\overline{A \cdot B}}$$

COMPSCI 210

14

## Using the DeMorgan Law

- How to implement any gate with two-input NAND (or NOR) gates?

$$\begin{aligned} A + B &= \overline{\overline{A + B}} \\ &= \overline{\bar{A} \cdot \bar{B}} \\ &= \overline{\overline{\overline{A \cdot 1} \cdot \overline{B \cdot 1}}} \end{aligned}$$

- Exercise: How to implement a three-input OR gate with two-input NAND and NOR gates?

COMPSCI 210

15

## Agenda

- Logic gates
- Simple logic circuits**
  - **Build combinational circuits to carry out simple operations, e.g. addition, selection, etc.**
  - **Build sequential circuits to store information, e.g. registers**

COMPSCI 210

16

## Building Functions from Logic Gates

### Combinational Logic Circuit

- output depends only on the current inputs
- stateless
- adder, decoder, etc.

### Sequential Logic Circuit

- output depends on the sequence of inputs (past and present)
- stores information (state) from past inputs
- register

COMPSCI 210

17

## Combinational Logic Circuit (1)

- The functionality of a combinational logic circuit can be represented using a truth table
- In the table below, A and B are the inputs of the circuit and C is the output of the circuit

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

COMPSCI 210

18

## Combinational Logic Circuit (2)

- The functionality of the circuit can be represented in terms of the inputs of the circuit using a logic expression
- The logic expression can be obtained from the truth table as below:
  - Identify the rows with output equal to 1
  - Use AND and NOT gates to make these rows' output equal to 1
  - Use OR gates to combine all the outputs from these rows
- From the logic expression, a logic circuit can be obtained

COMPSCI 210

19

## Combinational Logic Circuit (3)

- A and B are the inputs and C is the output
- The second and the third rows' outputs are 1
- How to write an expression written in terms of A and B to make the expression evaluate to 1 when A and B take the value in row 2/3
  - row 2 : (NOT A) AND B
  - row 3 : A AND (NOT B)
- How to write an expression to make C equal to 1 if either row 2 or 3 is 1
  - (row 2) OR (row 3)


A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

COMPSCI 210

20

## Decoder (1)

- A decoder is used to interpret the input value
  - $n$  input lines, i.e. there are  $2^n$  possible input pattern
  - $2^n$  output lines
  - exactly one output is 1 for each possible input pattern

 

COMPSCI 210

21

## Decoder (2)

- Truth table for output line “if  $AB=00$ ” is shown
- Only the first row’s output is 1
- The expression written in terms of A and B to make the expression evaluate to 1 when A and B take the value in row 1 is
  - (NOT A) AND (NOT B)
- Since row 1 is the only row with output equal to 1, the logic expression corresponds to the truth table is
  - (NOT A) AND (NOT B)


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

- The expression for the other output lines can be obtained similarly

COMPSCI 210

22

## Decoder (3)

 


COMPSCI 210

23

## Multiplexer (MUX) (1)

- A multiplexer can be used to control the information flowing through the system
  - $2^n$  input data lines,
  - one output data line
  - $n$ -bit selector lines
  - output equals to one of the input data lines, depending on the value presented to the selector lines

 

COMPSCI 210

24

## Multiplexer (MUX) (2)


- The AND gate can be used to control the flow of information
  - For an AND gate with two inputs, input and S
    - input can flow through the AND gate if S is 1, i.e. input AND S = input (if S = 1)
    - otherwise, input cannot flow through the AND gate
- For the MUX in the previous slide,

$$Out = A \cdot \bar{S}_1 \cdot \bar{S}_0 + B \cdot \bar{S}_1 \cdot S_0 + C \cdot S_1 \cdot \bar{S}_0 + D \cdot S_1 \cdot S_0$$

COMPSCI 210

25

## Multiplexer (MUX) (3)

 

COMPSCI 210

26

## Half Adder

- A half adder adds two bits together
  - 2 inputs, i.e. the two bits to be added
  - 2 outputs: sum and carry

$a_i$	$b_i$	$c_{i+1}$	$S_i$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

COMPSCI 210

27

## Full Adder (1)

- A number consists of multiple bits.
- When performs addition on bit  $i$ , we need to consider the carry in from bit  $i-1$
- A full adder
  - 3 inputs:  $a_i$ ,  $b_i$  and  $c_i$
  - 2 outputs:  $s_i$  and  $c_{i+1}$
  - $c_i$  is the carry in from bit position  $i-1$
  - $c_{i+1}$  is the carry out to bit position  $i+1$

$$\begin{array}{r}
 a_{n-1} \ a_{n-2} \ \dots \ a_1 \ a_0 \\
 + \ b_{n-1} \ b_{n-2} \ \dots \ b_1 \ b_0 \\
 + \ c_{n-1} \ c_{n-2} \ \dots \ c_1 \ 0 \\
 \hline
 s_{n-1} \ s_{n-2} \ \dots \ s_1 \ s_0
 \end{array}$$

COMPSCI 210

28


### Full Adder (2)

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

COMPSCI 210

29

### Four-bit Adder

 

COMPSCI 210

30

### Sequential Circuit


- A sequential circuit can store information
- It is useful for building “memory” elements
- We are going to learn
  - Simple Storage Elements, i.e. RS latch and D latch
  - Building registers and memory

COMPSCI 210

31
 
### R-S Latch

R is used to “reset” or “clear” the element – set it to zero.  
 S is used to “set” the element – set it to one.



If both R and S are one, out retains the current value.

- “quiescent” state -- holds its previous value
- note: if a is 1, then b is 0, and vice versa

COMPSCI 210

32

### Clearing the R-S latch

Suppose we start with output = 1, then change R to zero.

Output changes to zero.

Then set R=1 to "store" value in quiescent state.

COMPSCI 210 33

### Setting the R-S Latch

Suppose we start with output = 0, then change S to zero.

Output changes to one.

Then set S=1 to "store" value in quiescent state.

COMPSCI 210 34

### R-S Latch Summary

- R = S = 1**
  - hold current value in latch
- S = 0, R=1**
  - set value to 1
- R = 0, S = 1**
  - set value to 0
- R = S = 0**
  - both outputs equal one
  - final state determined by electrical properties of gates
  - **Don't do it!**





COMPSCI 210 35

### Gated D-Latch

Two inputs: D (data) and WE (write enable)

- when WE = 0, latch holds previous value
  - S = R = 1
- when WE = 1, latch is set to value of D
  - S = NOT(D), R = D

COMPSCI 210 36

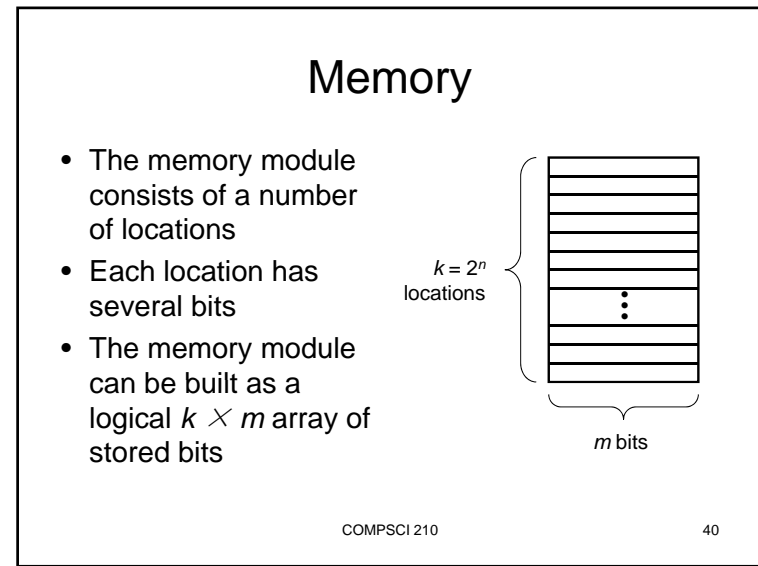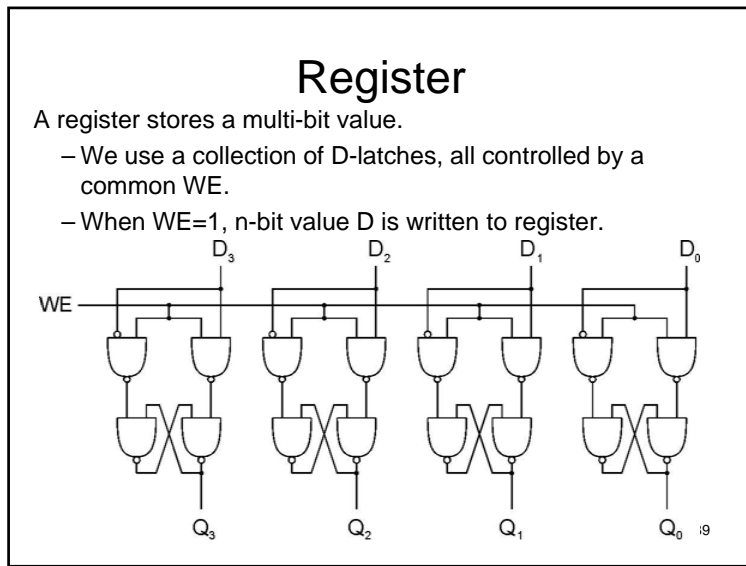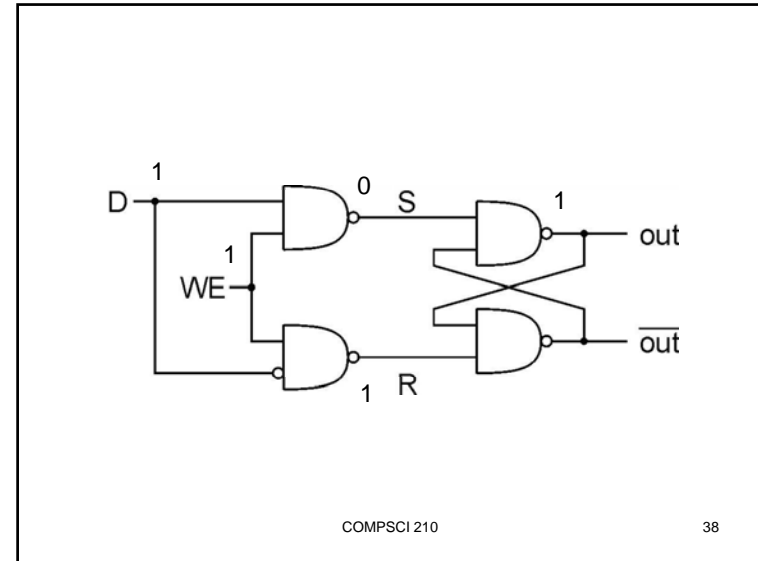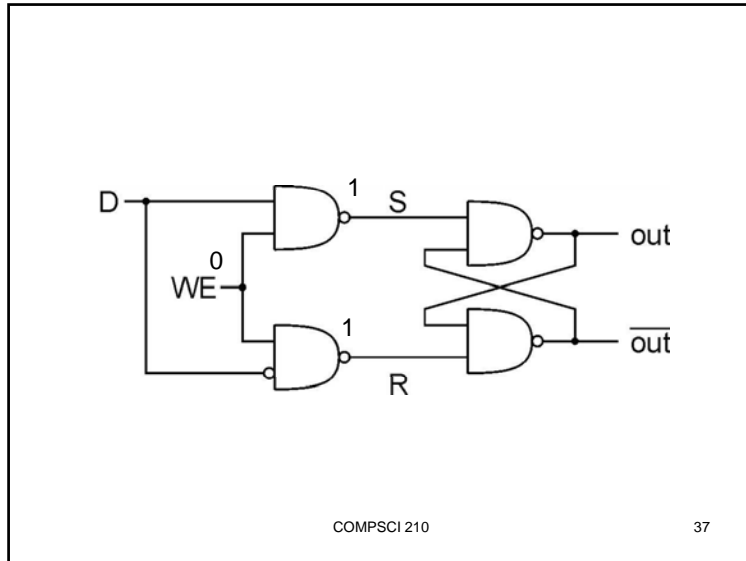


### Building a 4 x 1-bit Memory (1)

- Each location consists of 1 bit
  - Each bit is a gated D-latch
- There are 4 locations
- When read from or write to a location, the address of the location is given
- How to read from a given location
  - MUX:
    - the value of each location is the input of the MUX,
    - the address of the location are the selection line
    - the output of the MUX is the value of the location being read
- How to write to a given location
  - Decoder:
    - the address of the location is the input to the decoder
    - each output line of the decoder connects to the WE line of one of the locations

COMPSCI 210

41

### Building a 4 x 1-bit Memory (2)

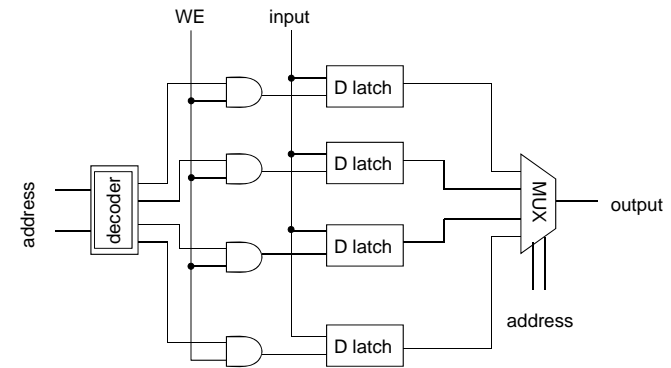

COMPSCI 210

42

## reviews

- How the logic gates behave
  - NOT, NAND, NOR, OR, AND
- How to use the DeMorgan's Law to convert a logic expression that contains NAND/NOR operators only
- The differences between combinational and sequential circuits
- Write a logic expression to represent the functionalities specified in a truth table
- RS and D latch
  - How they work
  - Build storage devices using the latches

COMPSCI 210

43