

Computer Science 210
Computer Systems 1
Lecture Notes

Lecture 7
Digital Logic Structures

Credits: Slides prepared by Gregory T. Byrd, North Carolina State University

Building Functions from Logic Gates

Combinational Logic Circuit

- output depends only on the current inputs
- stateless

Sequential Logic Circuit

- output depends on the sequence of inputs (past and present)
- stores information (state) from past inputs

We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.


CS210

2

Decoder

• n inputs, 2^n outputs

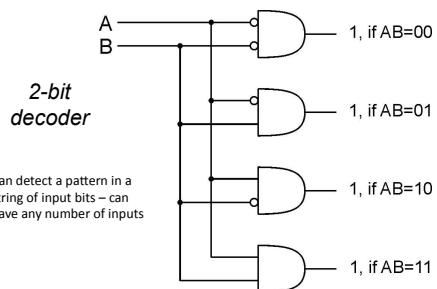- exactly one output is 1 (true) for each possible input pattern



3

Two Variables

16 possible unique functions

A	B	f ₀	f ₁	f ₂	f ₃	f ₄	f ₅	f ₆	f ₇	f ₈	f ₉	f ₁₀	f ₁₁	f ₁₂	f ₁₃	f ₁₄	f ₁₅
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

ZERO → f₀ f₁ f₂ f₃ f₄ f₅ f₆ f₇ f₈ f₉ f₁₀ f₁₁ f₁₂ f₁₃ f₁₄ f₁₅ ONE

XOR A ⊕ B
 AND A ∧ B
 B
 A ∧ B
 A ⊕ B
 XNOR A ⊕ B
 A
 OR A ∨ B
 NOR $\overline{A \vee B} = \overline{A} \wedge \overline{B}$
 NAND $\overline{A \wedge B}$
 De Morgan's Law

CS210 4

Truth Table for Function F

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


XOR
 F is True if 1 or 3 inputs are true
 F is False if zero or 2 inputs are true
 More generally F is true if an odd number of inputs are true

CS210

5

Creating a Circuit from a Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

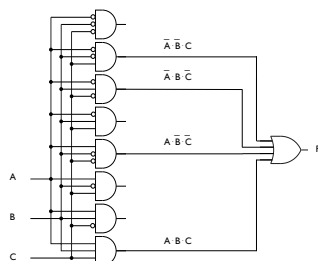


CS210

6

Multiplexer (MUX)

n -bit selector and 2^n inputs, one output


– output equals one of the inputs, depending on selector S_1 & S_2

 

CS210

7

Four-bit Adder

 


This is a ripple-carry adder – operates from right to left

CS210

8

Four-bit Adder

 


Each full adder is implemented with an XOR gate with three inputs A, B & C
The output S is True (1) when an odd number of inputs is true
The C_{out} is True (1) if 2 or 3 inputs are true (the majority)

CS210

9

Full Adder

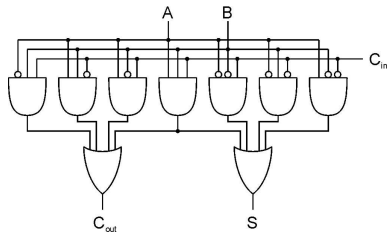Add two bits and carry-in,
produce one-bit sum and carry-out




A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CS210

10

Full Adder

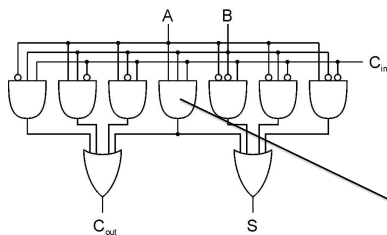Add two bits and carry-in,
produce one-bit sum and carry-out



A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


CS210

11

Logical Completeness

•Can implement ANY truth table with AND, OR, NOT

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. AND combinations
that yield a "1" in the
truth table.

2. OR the results
of the AND gates.

CS210

12

Logical Completeness

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0


Can implement ANY truth table with just NAND or NOR

We might not want to for reasons of simplicity

CS210

13

DeMorgan's Law

 


CS210

14

De Morgan's Theorem

 Using Only NAND gates to create a NOR gate



NOR gate constructed using only NAND gates


credit: http://en.wikipedia.org/wiki/NOR_gate

CS210

15

De Morgan's Theorem

 Using Only NOR gates to create a NAND gate



credit: http://en.wikipedia.org/wiki/NOR_gate

CS210

16

Combinational vs. Sequential

Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- *example*: ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building “memory” elements and “state machines”


CS210

17

SR-Latch: Simple Storage Element Flip-Flop

S is used to “set” the element – set output Q to one

 R is used to “reset” or “clear” the element – set output Q to zero



SR latch operation		
S	R	Action
0	0	Restricted combination
0	1	Q = 1
1	0	Q = 0
1	1	No Change

This gives us the ability to store a bit (either 0 or 1)


Watch the video <http://youtu.be/ti5jD7Q7B5A>

CS210

18

SR-Latch: Simple Storage Element Flip-Flop

 S is used to "set" the element – set output Q to one
R is used to "reset" or "clear" the element – set output Q to zero



Characteristic table			
S	R	Q_{next}	Action
0	0	Q	hold state
0	1	0	reset
1	0	1	set
1	1	X	not allowed

This gives us the ability to store a bit (either 0 or 1)

CS210

19