

Computer Science 210

Computer Systems 1

Lecture 9

Finite State Machines

Credits: Slides prepared by Gregory T. Byrd, North Carolina State University

Finite State Machine

A description of a system with the following components:

1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what determines each external **output value**


Often described by a state diagram.

- Inputs trigger state transitions.
- Outputs are associated with each state (or with each transition).

CS210 2

The Clock

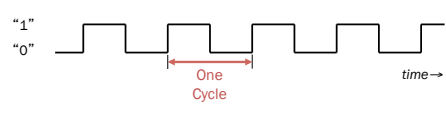Frequently, a **clock circuit** triggers transition from one state to the next.



At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs

CS210 3


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state

Storage elements

- Maintain state representation

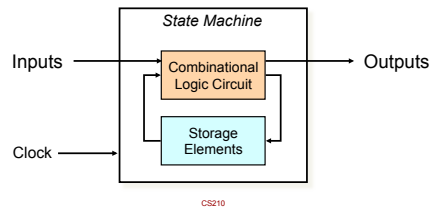


CS210

4

Storage: Master-Slave Flip flop

A pair of gated D-latches,
to isolate *next* state from *current* state.

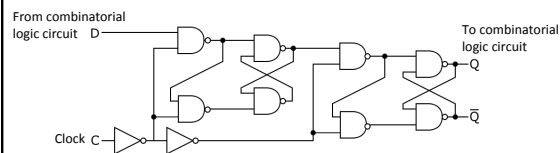


CS210

5

Storage: Master-Slave Flip flop

Master-slave edge triggered D flip-flop

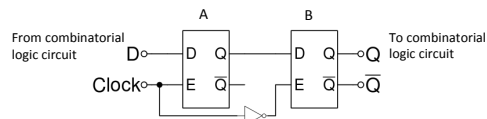

During 1st phase (clock=1),
previously-computed state in A
becomes *current* state in Latch B
and is sent to the logic circuit.

During 2nd phase (clock=0),
next state, computed by
logic circuit, is stored in
Latch A.

CS210


6

Flip-Flops

- Many types
- Look at

[http://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))

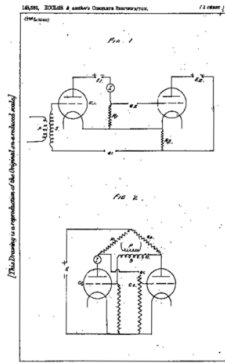Flip-flop schematics
from the Eccles and
Jordan patent filed 1918



Storage

- Each master-slave flipflop stores one state bit.
- The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).

• Examples:

- Sequential lock
 - Four states – two bits
- Basketball scoreboard
 - 7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...


CS210

8

Complete Example

• A blinking traffic sign

- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)

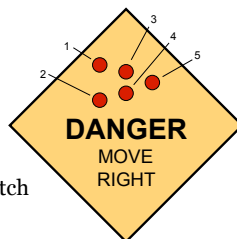


CS210

9



Traffic Sign Logic

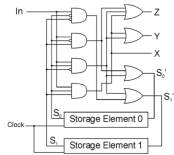

Of course our traffic sign controller has been implemented in hardware.

If wanted to change its operation we can't.

Implementing a generic controller in hardware that could be controlled by software would give us more flexibility but would be more complicated.

CS210

13

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 on next slide.

•Combinational Logic

- Decoders – convert S into control signals
- Multiplexers – select inputs and outputs
- ALU (Arithmetic and Logic Unit) – operations on data


•Sequential Logic

- State machine – coordinate control signals and data movement
- Registers and latches – storage elements

CS210

14

LC-3 Data Path

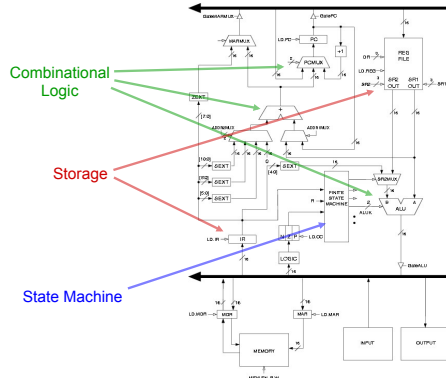

15